 


Report for Dice Game



Question1:

The FSM of the flow chart is as follows



Question 2:

The Simulation are as follows:

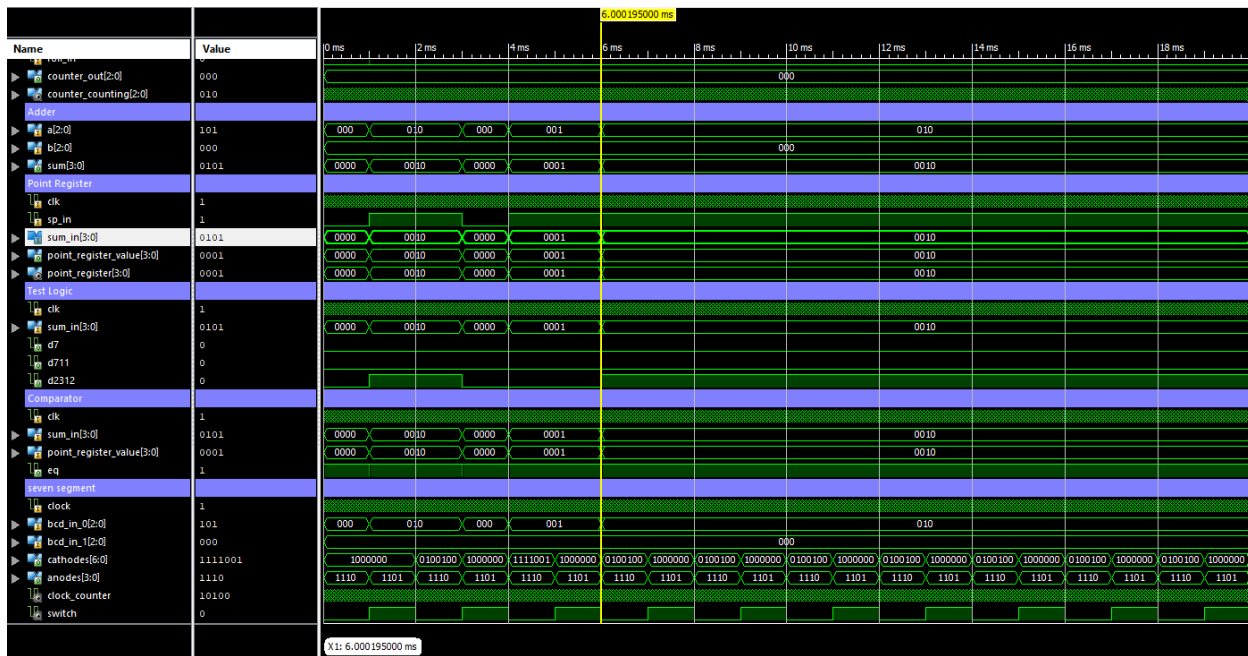 



Win and Lose conditions

The Top Module is as follows:

```

-----
-- Company:
-- Engineer:
--
-- Create Date: 21:32:06 10/25/2024
-- Design Name:
-- Module Name: top - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using

```

```

-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity top is
    Port(
        clock : in std_logic;
        Reset : in std_logic;
        Rb : in std_logic;
        Win : out std_logic := '0';
        Lose : out std_logic := '0';
        cathodes_out : out std_logic_vector(6 downto 0) := (others => '0');
        anodes_out : out std_logic_vector(3 downto 0) := (others => '1')
    );
end top;

architecture Behavioral of top is

    component Edge_Detector
        Port(
            CLK_SYS : in std_logic;
            BUTTON_IN : in std_logic;
            PULSE : out std_logic
        );
    end component;

    component Control is
        Port(
            clk : in std_logic;
            Rb : in std_logic;
            Reset : in std_logic;
            D7_in : in std_logic;
            D711_in : in std_logic;
            D2312_in : in std_logic;
            Eq_in : in std_logic;
            Roll : out std_logic;
            Win : out std_logic;
            Lose : out std_logic;
            Sp : out std_logic
        );
    end component;

    component onetosix_counter
        Port(

```

```

        clk : in std_logic;
        reset : in std_logic;
        Roll_in : in std_logic;
        counter_out : out std_logic_vector(2 downto 0)
    );
end component;

component clock_divider is
generic(
    FPGA_CLK_FREQUENCY : integer := 100000000;
    REQUIRED_FREQUENCY : integer := 50000000
);
Port (
    clock_in : in STD_LOGIC;
    clock_out : out STD_LOGIC
);
end component;

component Adder
Port (
    A : in STD_LOGIC_VECTOR(2 downto 0); -- 4-bit input A
    B : in STD_LOGIC_VECTOR(2 downto 0); -- 4-bit input B
    SUM : out STD_LOGIC_VECTOR(3 downto 0) -- 5-bit Sum Output
);
end component;

component point_register
Port(
    clk : in STD_LOGIC;
    Sp_in : in STD_LOGIC;
    SUM_IN : in std_logic_vector(3 downto 0);
    point_register_value : out std_logic_vector(3 downto 0)
);
end component;

component comparator
Port(
    clk : in std_logic;
    sum_in : in std_logic_vector(3 downto 0);
    point_register_value : in std_logic_vector(3 downto 0);
    Eq : out std_logic
);
end component;

component Test_Logic
Port(
    clk : in std_logic;
    sum_in : in std_logic_vector(3 downto 0);

```

```

        D7 : out std_logic;
        D711 : out std_logic;
        D2312 : out std_logic
    );
end component;

component bcdto7seg
    Port (
        clock : in std_logic;
        bcd_in_0 : in std_logic_vector (2 downto 0);
        bcd_in_1 : in std_logic_vector (2 downto 0);
        cathodes : out std_logic_vector (6 downto 0);
        anodes : out std_logic_vector (3 downto 0)
    );
end component;

signal start_button : std_logic := '0';
signal reset_button : std_logic := '0';
signal Roll_out : std_logic := '0';
signal Win_out : std_logic := '0';
signal Lose_out : std_logic := '0';
signal counter_one_out : std_logic_vector (2 downto 0) := (others => '0');
signal counter_two_out : std_logic_vector (2 downto 0) := (others => '0');
signal clock_divided_1 : std_logic := '0';
signal clock_divided_2 : std_logic := '0';
signal Sum_out : std_logic_vector (3 downto 0) := (others => '0');
signal point_register_val : std_logic_vector (3 downto 0) := (others => '0');
signal Eq_out : std_logic := '0';
signal D7_out : std_logic := '0';
signal D711_out : std_logic := '0';
signal D2312_out : std_logic := '0';
signal Sp_out : std_logic := '0';
begin

    uut : Edge_Detector
    port map(
        CLK_SYS => clock,
        BUTTON_IN => Rb,
        PULSE => start_button
    );

    uut2 : Edge_Detector
    port map(
        CLK_SYS => clock,
        BUTTON_IN => Reset,
        PULSE => reset_button
    );

```

```

 uut3 : Control
port map(
    clk => clock,
    Rb => start_button,
    Reset => reset_button,
    D7_in => D7_out,
    D711_in => D711_out,
    D2312_in => D2312_out,
    Eq_in => Eq_out,
    Roll => Roll_out,
    Win => Win,
    Lose => Lose,
    Sp => Sp_out

);

-- uut4 : clock_divider
-- generic map(
--     FPGA_CLK_FREQUENCY => 100000000,
--     REQUIRED_FREQUENCY => 100000000
-- )
-- port map(
--     clock_in => clock,
--     clock_out => clock_divided_1
-- );

 uut5 : onetosix_counter
port map(
    clk => clock,
    reset => reset_button,
    Roll_in => Roll_out,
    counter_out => counter_one_out

);

 uut6 : clock_divider
generic map(
    FPGA_CLK_FREQUENCY => 100000000,
    REQUIRED_FREQUENCY => 50000000
)
port map(
    clock_in => clock,
    clock_out => clock_divided_2

);

 uut7 : onetosix_counter
port map(
    clk => clock_divided_2,
    reset => reset_button,

```

```

        Roll_in => Roll_out,
        counter_out => counter_two_out
    );

    uut8 : Adder
    port map(
        A => counter_one_out,
        B => counter_two_out,
        SUM => Sum_out
    );

    uut9 : point_register
    port map(
        clk => clock,
        Sp_in => Sp_out,
        SUM_IN => Sum_out,
        point_register_value => point_register_val
    );

    uut10 : comparator
    port map(
        clk => clock,
        sum_in => Sum_out,
        point_register_value => point_register_val,
        Eq => Eq_out
    );

    uut11 : Test_Logic
    Port map(
        clk  => clock,
        sum_in  => Sum_out,
        D7  => D7_out,
        D711  => D711_out,
        D2312 => D2312_out
    );

    uut12 : bcdto7seg
    Port map (
        clock => clock,
        bcd_in_0 => counter_one_out,
        bcd_in_1 => counter_two_out,
        cathodes => cathodes_out,
        anodes => anodes_out
    );

```

end Behavioral;

Question 3:

The Constraint Requirements for the FPGA of Nexys 3 are as follows:

```
## This file is a general .ucf for Nexys3 rev B board
## To use it in a project:
## - remove or comment the lines corresponding to unused pins
## - rename the used signals according to the project

##Clock signal
Net "clock" LOC=V10 | IOSTANDARD=LVCMOS33;

## 7 segment display
Net "cathodes_out(0)" LOC = T17 | IOSTANDARD = LVCMOS33; #Bank = 1, pin name =
IO_L51P_M1DQ12, Sch name = CA
Net "cathodes_out(1)" LOC = T18 | IOSTANDARD = LVCMOS33; #Bank = 1, pin name =
IO_L51N_M1DQ13, Sch name = CB
Net "cathodes_out(2)" LOC = U17 | IOSTANDARD = LVCMOS33; #Bank = 1, pin name =
IO_L52P_M1DQ14, Sch name = CC
Net "cathodes_out(3)" LOC = U18 | IOSTANDARD = LVCMOS33; #Bank = 1, pin name =
IO_L52N_M1DQ15, Sch name = CD
Net "cathodes_out(4)" LOC = M14 | IOSTANDARD = LVCMOS33; #Bank = 1, pin name = IO_L53P, Sch
name = CE
Net "cathodes_out(5)" LOC = N14 | IOSTANDARD = LVCMOS33; #Bank = 1, pin name = IO_L53N_VREF,
Sch name = CF
Net "cathodes_out(6)" LOC = L14 | IOSTANDARD = LVCMOS33; #Bank = 1, pin name = IO_L61P, Sch
name = CG
#Net "cathodes_out(7)" LOC = M13 | IOSTANDARD = LVCMOS33; #Bank = 1, pin name = IO_L61N, Sch
name = DP

Net "anodes_out(0)" LOC = N16 | IOSTANDARD = LVCMOS33; #Bank = 1, pin name =
IO_L50N_M1UDQSN, Sch name = AN0
Net "anodes_out(1)" LOC = N15 | IOSTANDARD = LVCMOS33; #Bank = 1, pin name =
IO_L50P_M1UDQS, Sch name = AN1
Net "anodes_out(2)" LOC = P18 | IOSTANDARD = LVCMOS33; #Bank = 1, pin name =
IO_L49N_M1DQ11, Sch name = AN2
Net "anodes_out(3)" LOC = P17 | IOSTANDARD = LVCMOS33; #Bank = 1, pin name =
IO_L49P_M1DQ10, Sch name = AN3

## Leds
Net "Win" LOC = U16 | IOSTANDARD = LVCMOS33; #Bank = 2, pin name = IO_L2P_CMPCLK, Sch name
= LD0
Net "Lose" LOC = V16 | IOSTANDARD = LVCMOS33; #Bank = 2, pin name = IO_L2N_CMPMOSI, Sch
name = LD1

## Switches
```

```
Net "Rb" LOC = T10 | IOSTANDARD = LVCMOS33; #Bank = 2, pin name = IO_L29N_GCLK2, Sch name = SW0
Net "Reset" LOC = T9 | IOSTANDARD = LVCMOS33; #Bank = 2, pin name = IO_L32P_GCLK29, Sch name = SW1
```

These includes 2 switches, 2LED and 2 seven segments which are refreshing at 1ms response time.